

# Single Cycle RISC\_V Processor REPORT

**Ziad Ahmed**

8//27//2024

—

RTL & Functional\_Verfication

—

[GitHub REPO](#)

ITI

---

# Specs



## Verilog Design of Single-Cycle RISC-V Processor

- 1-Design a single-cycle processor datapath and control logic.
- 2-Run and debug logic simulations.
- 3-Your processor should implement the following subset of RV32I instruction set:
  - a. **R-Type**: add, sub, and, or
  - b. **I-Type**: addi, andi, ori, lw, jalr
  - c. **B-Type**: beq, bne
  - d. **J-Type**: jal
  - e. **S-Type**: sw
- 4-Use 1 ns clock period in your testbench.
- 5-Note that reading register-file/memory data is combinational, but writing is clocked.
- 6-The top module should be divided into two main modules: datapath and control logic. The Instruction and data memories should be connected to the top module in the testbench.
- 7-For simplicity, assume that the instruction memory is a 1kB word-addressable ROM and the data memory is a 1kB word-addressable RAM, i.e., you will only connect bits 9 to 2 in the address bus.
- 8-Use Venus to generate the machine code for an arbitrary sample program.
- 9-Then implement a simple cache system and integrate it with the RISC-V processor.
- 10-Re run your assembly code and compare simulation


**Hint:** Read Section 7.3 **Single-Cycle Processor** in the textbook (DDCA by Harris and Harris) as it will be a good starting point.

### **Reference Cache-controller:**


- 1- <https://ocw.mit.edu/courses/6-004-computation-structures-spring-2017/pages/c14/>
- 2- <https://slidetodoc.com/cache-performance-metrics-miss-rate-fraction-of-memory-2/>

وَمَا أَوْتَيْتُمْ مِنَ الْعِلْمِ إِلَّا قَلِيلًا

## Block Diagram for RISC V Processor

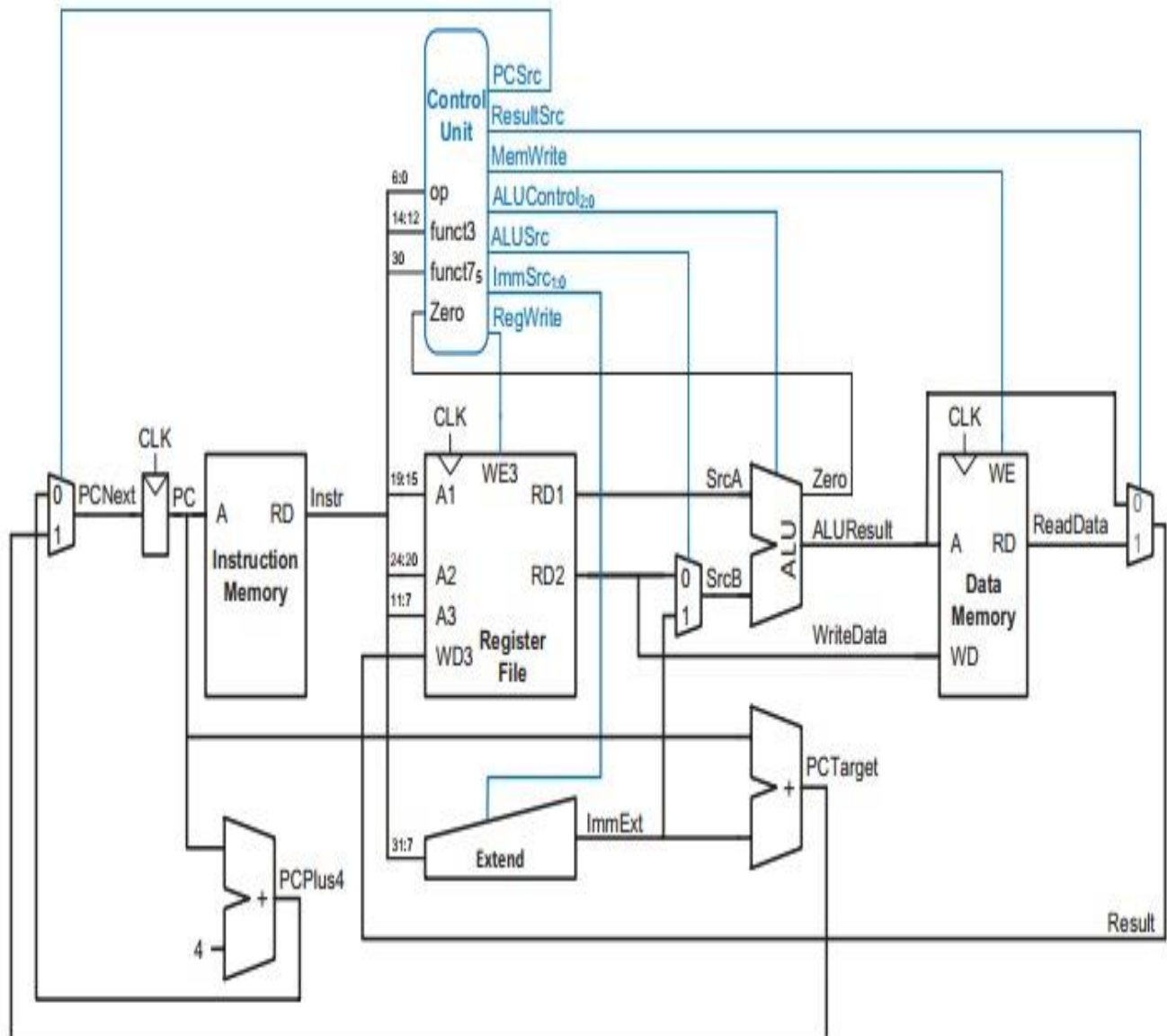


# RISC-V Processor Architecture

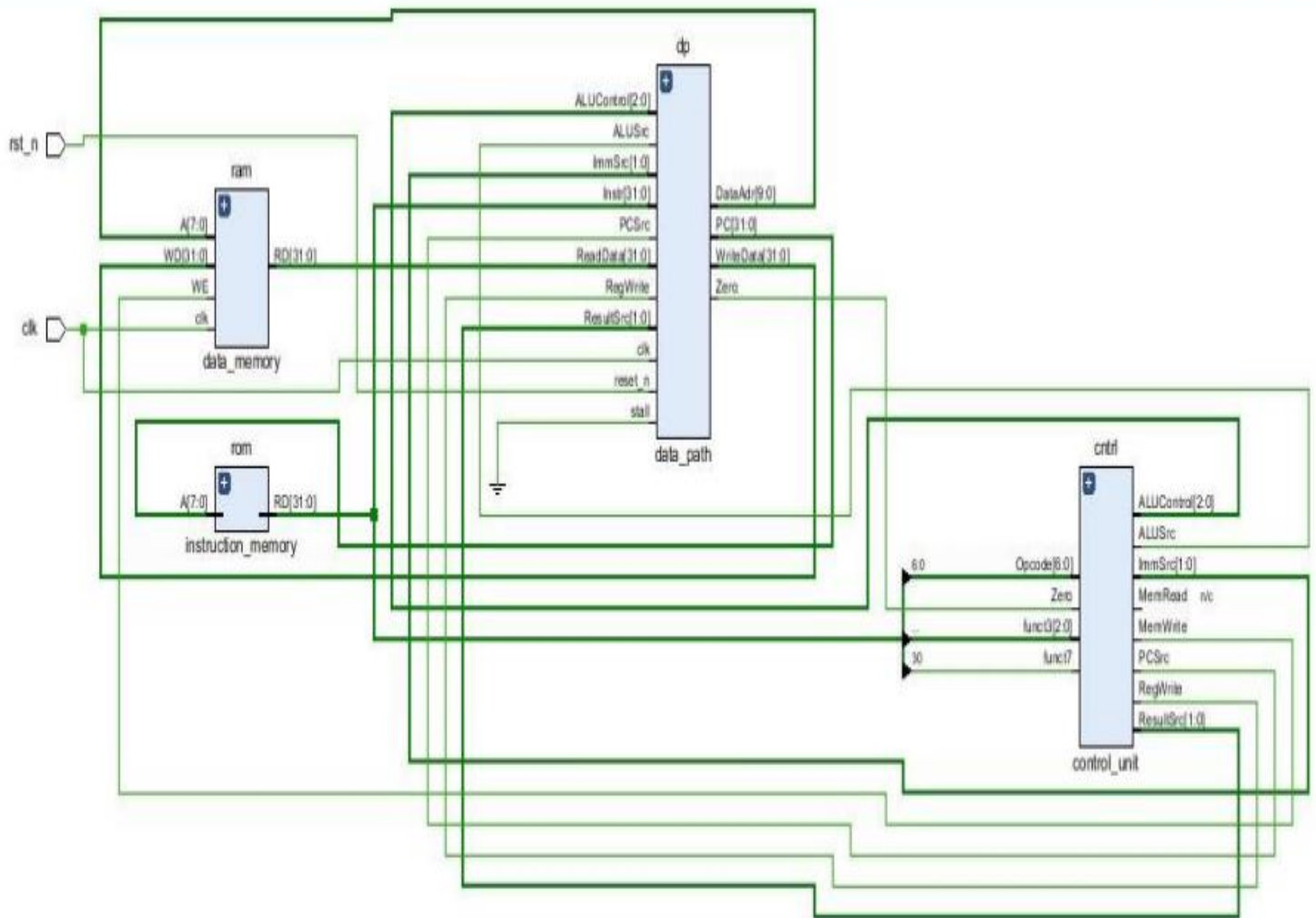




# Main Blocks for The System

## Control unit

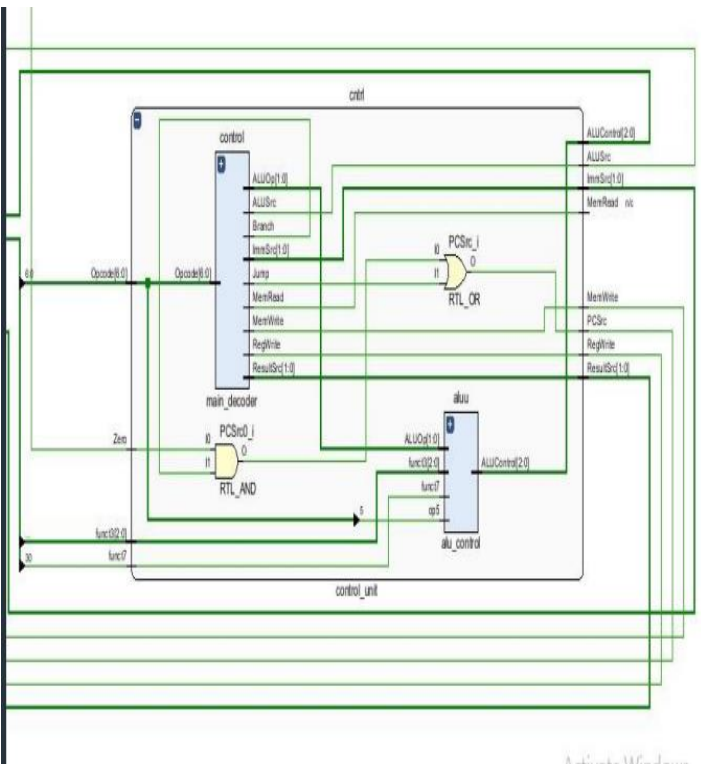

## Datapath

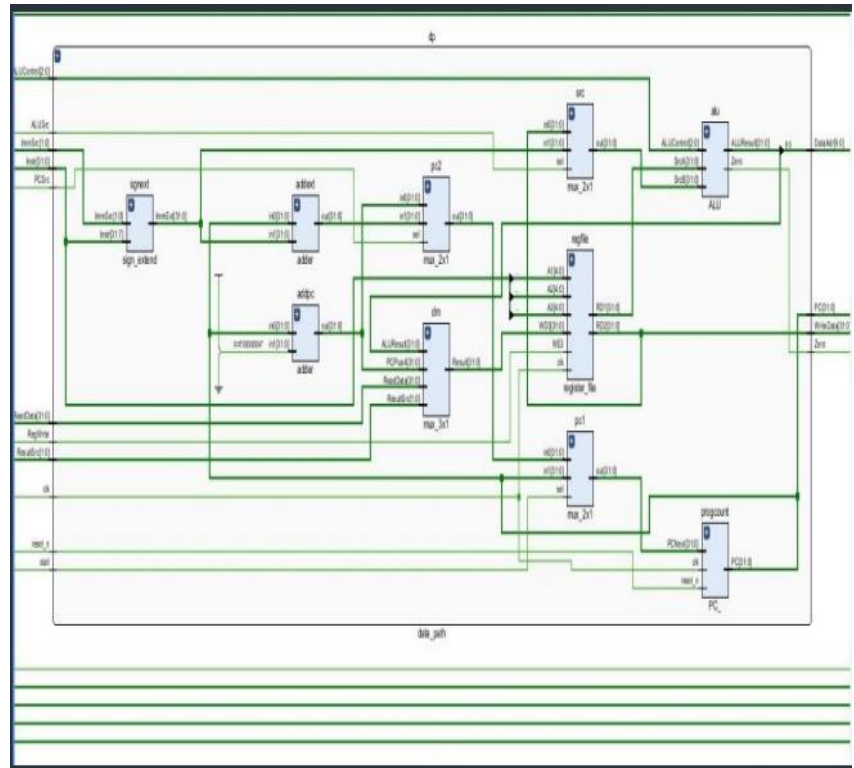

## Sample assembly program

```
##### Sample assembly program #####

    ### S Format Instruction  sw

sw x2, 4(x1)          ##### Machine Code == 32'b00000000001000001010001000100011

    ### R Format Instruction  add

add x3, x1, x2        ##### Machine Code == 32'b00000000001000001000000110110011

    ### I Format Instruction  addi

addi x4, x1, 10       ##### Machine Code == 32'b00000000101000001000001000010011

    ### I Format Instruction  lw

lw x7, 4(x1)          ##### Machine Code == 32'b00000000000000101010001110000011


    ### B Format Instruction  beq

beq x1, x1, label     ##### Machine Code == 32'b00000000000100001000000001100011
```


## Transcript Snip Showing Passed Test Cases

```
# TESTING sw Instruction (sw x2, 4(x1)) Storing value inside REG2 = 2 into Location 1 in the Memory
# Test Case Passed and the Value stored in REG 2 =      2  at Time      900
# TESTING R Instruction Add operation (add x3, x1, x2)  REG3 == 1 + 2
# Test Case Passed and the Value stored in REG 3 =      3  at Time     1000
# TESTING I Instruction Addi operation (addi x4, x1, 10) REG4 == 1 + 10
# Test Case Passed and the Value stored in REG 4 =     11  at Time     1100
# TESTING lw Instruction Load operation (lw x7, 0(x1)) loading From Location 1 in The Memory = 2  Into REG7
# Test Case Passed and the Value stored in REG 7 =      2  at Time     1200
# TESTING BEQ Instruction (beq x1, x1, label) Branching into label
# Test Case Passed and the Value For PC =     12  at Time     1300
# ** Note: $stop    : E:/Digital Projects/Single_RISC_V_Project/SINGLE_RISC_V_TB.v(81)
# Time: 1600 ns  Iteration: 0  Instance: /SINGLE_RISC_V_TB
```

**WAVE\_FORM FOR SW instruction**

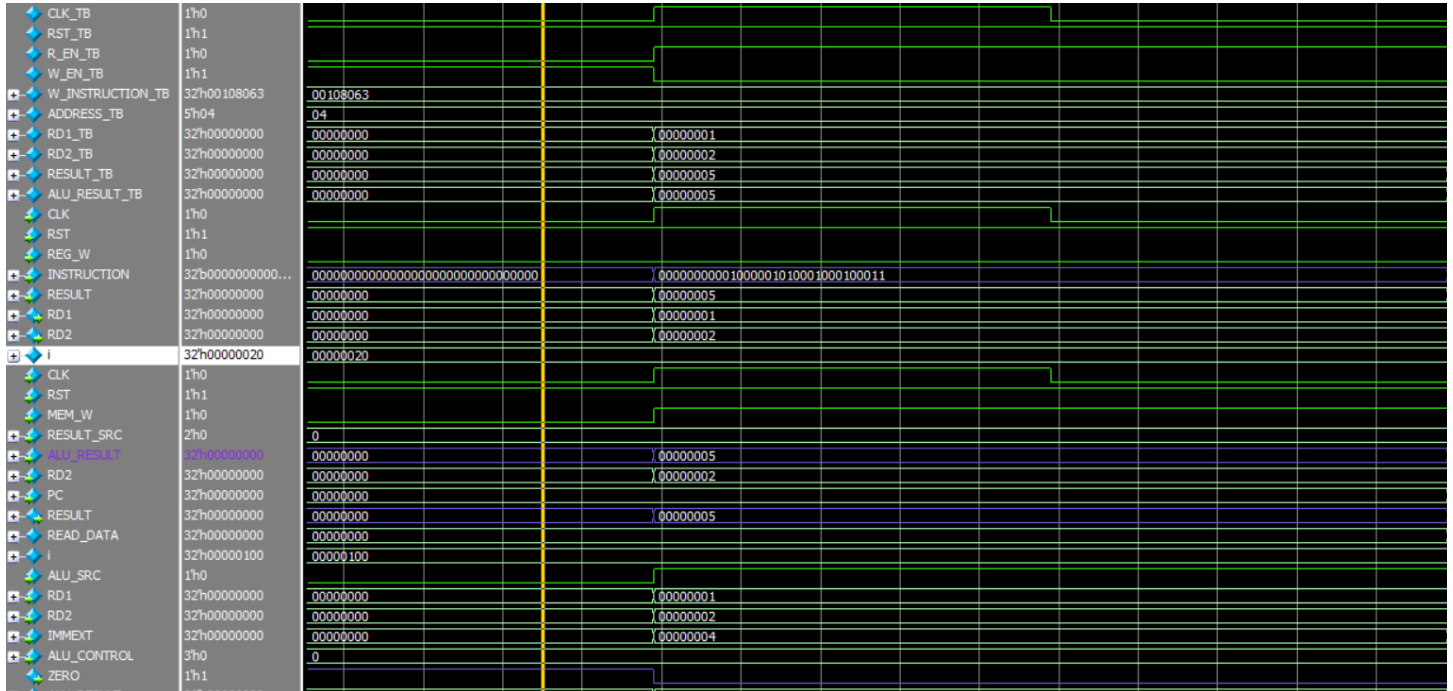
$$sw \ x2, 4(x1)$$

 
Value Stored In location 1 In the Mem (Should = Value inside REG2 which is 2 )



## WAVE\_FORM FOR ADD instruction

add x3, x1, x2

 


Value Stored In REG3 In the REG\_FILE (Should = Value inside REG1 + REG2 = 1 + 2 )

Memory Data - /SINGLE_RISC_V_TB/DUT/REG_FILE/REGISTERS - Default							
0000001f	0000001f	0000001e	0000001d	0000001c	0000001b	0000001a	00000019
00000018	00000018	00000017	00000016	00000015	00000014	00000013	00000012
00000011	00000011	00000010	0000000f	0000000e	0000000d	0000000c	0000000b
0000000a	0000000a	00000009	00000008	00000007	00000006	00000005	00000004
00000003	00000003	00000002	00000001	00000000			
ffffffffc							



## WAVE\_FORM FOR ADDI instruction

addi x4, x1, 10

 


Value Stored In REG4 In the REG\_FILE (Should = Value inside REG1 + 10 = 1 + 10 )

Memory Data - /SINGLE_RISC_V_TB/DUT/REG_FILE/REGESTERS - Default							
0000001f	0000001f	0000001e	0000001d	0000001c	0000001b	0000001a	00000019
00000018	00000018	00000017	00000016	00000015	00000014	00000013	00000012
00000011	00000011	00000010	0000000f	0000000e	0000000d	0000000c	0000000b
0000000a	0000000a	00000009	00000008	00000007	00000006	00000005	0000000b
00000003	00000003	00000002	00000001	00000000			
fffffffc							

## WAVE\_FORM FOR LW instruction

lw x7, 4(x1)

 

Value Stored In REG7 In REG\_File(Should = Location 1 In the Memory = 2)

Memory Data - /SINGLE_RISC_V_TB/DUT/REG_FILE/REGESTERS - Default							
0000001f	0000001f	0000001e	0000001d	0000001c	0000001b	0000001a	00000019
00000018	00000018	00000017	00000016	00000015	00000014	00000013	00000012
00000011	00000011	00000010	0000000f	0000000e	0000000d	0000000c	0000000b
0000000a	0000000a	00000009	00000008	00000002	00000006	00000005	0000000b
00000003	00000003	00000002	00000001	00000000			
fffffffc							

## WAVE\_FORM FOR BEQ instruction

beq x1, x1, label

Value Stored In PC In PC\_COUNTER(Should = PC\_TARGET = 0X000C) && PCSRC = 1

